

CSC34300

Lecture 05: Simple FSM Implementation

Instructor: Zheng Peng


Computer Science Department

City College of New York

Introduction


- FSM: Finite State Machine
 - The term “finite” refers to the fact that the number of states the circuit can display is finite
 - Sequential Circuit
 - Output depends not only on current input but also on past input values
 - Store information between operations
 - Outputs from the system are usually taken as new inputs (usually with delay), or “feedbacks”

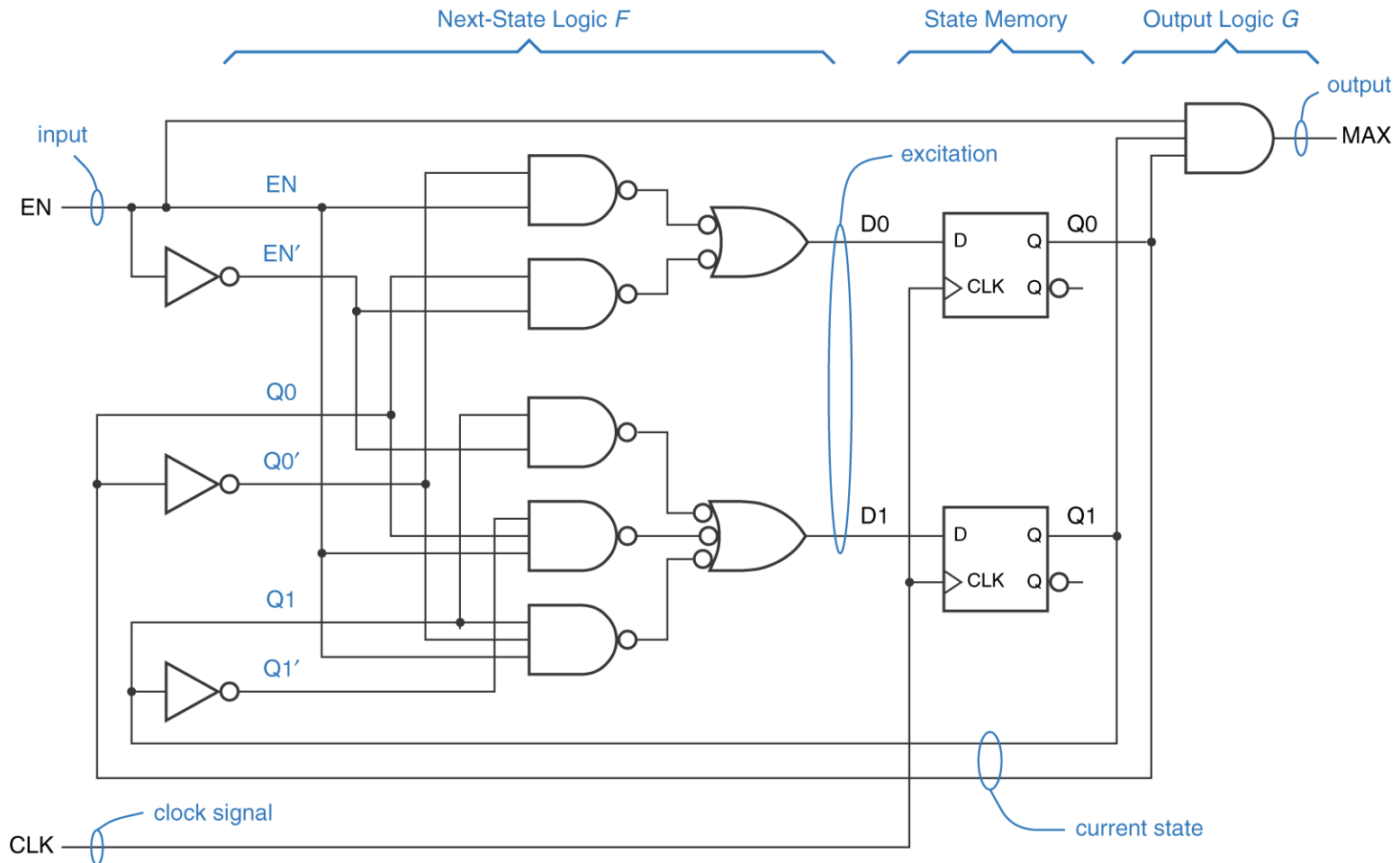A State Machine with Two Positive-edge-triggered D Flip-Flop




A State Machine with Two Positive-edge-triggered D Flip-Flop

- The corresponding state diagram

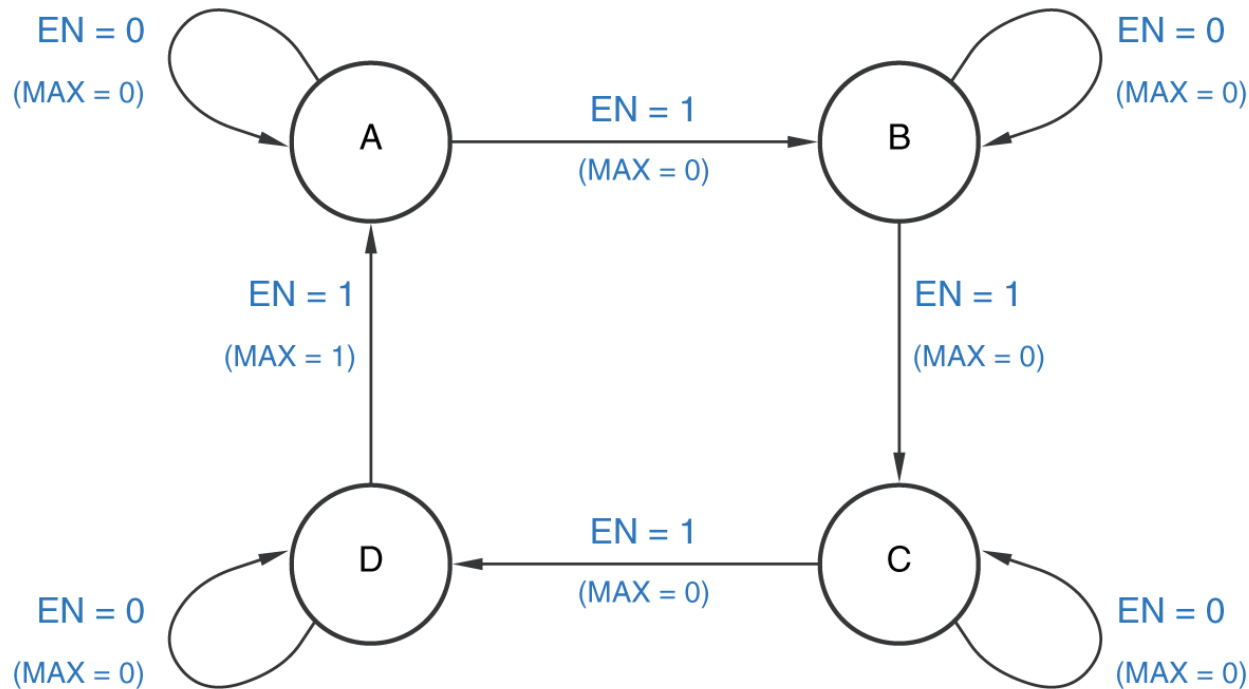


S	EN	
	0	1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1
S*, MAX		

 VHDL FSM Implementation Example: Traffic Lights Control




VHDL FSM Implementation Example: Traffic Lights Control

- State diagram

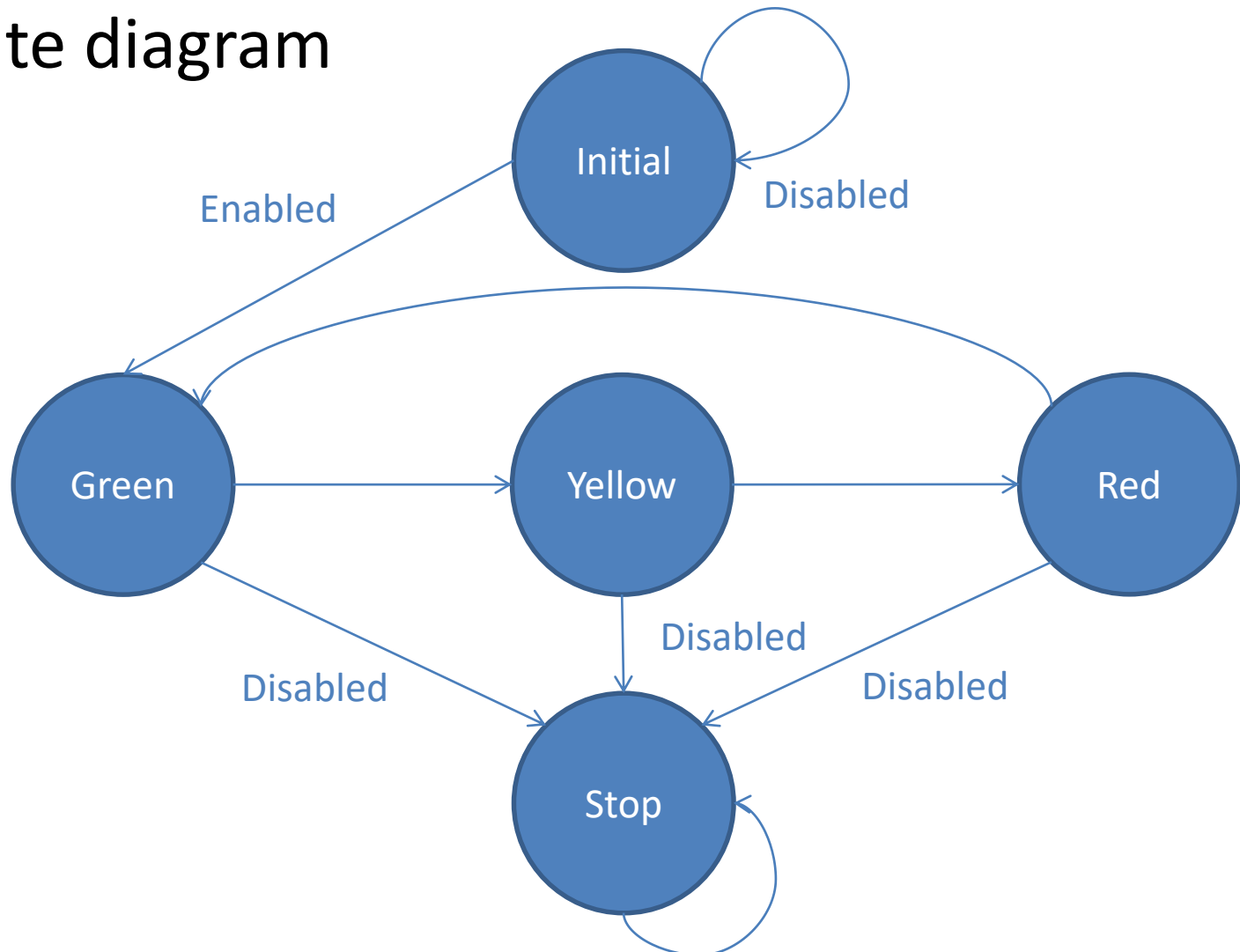


VHDL FSM Implementation Example: Traffic Lights Control

- Module design

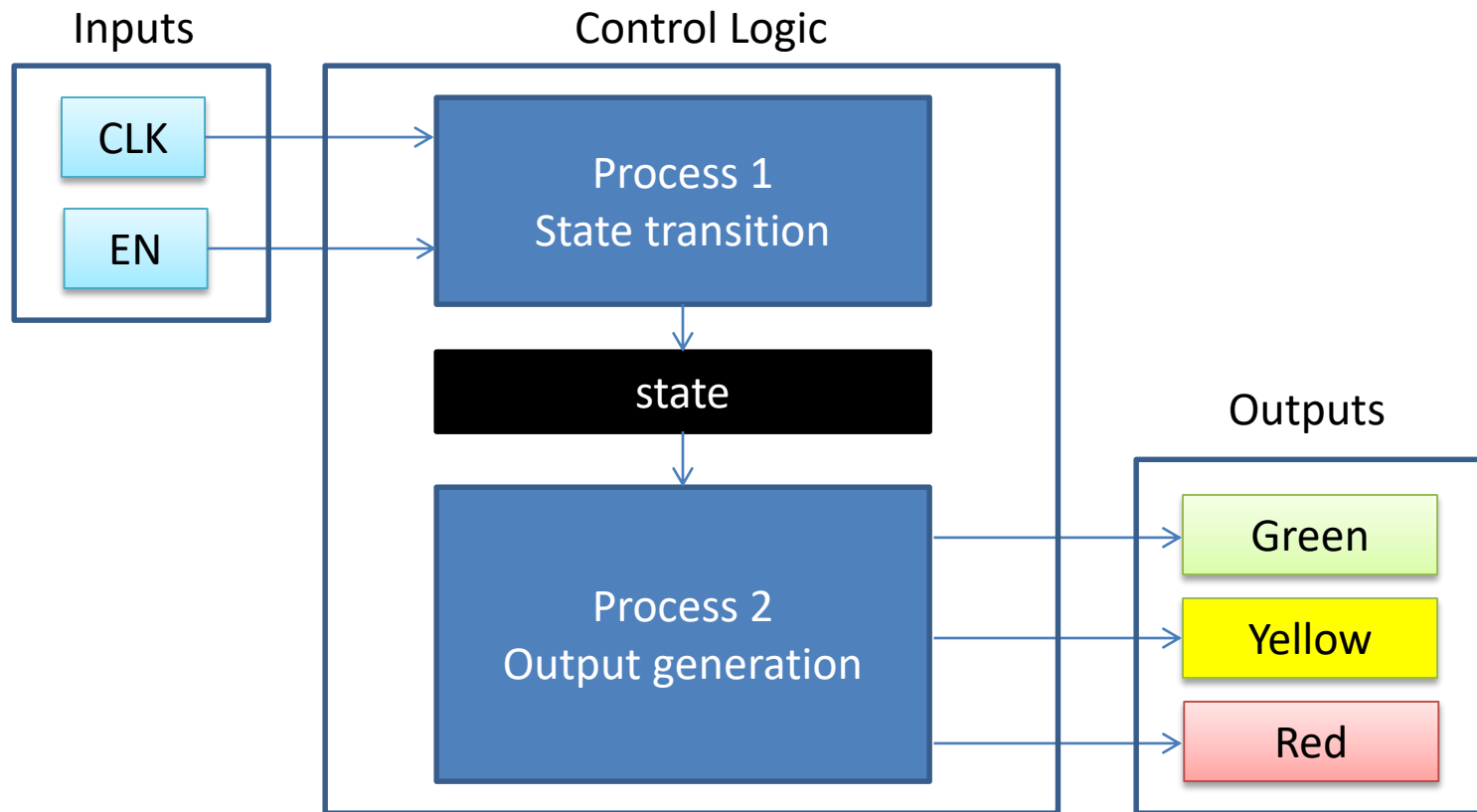

VHDL FSM Implementation Example: Traffic Lights Control

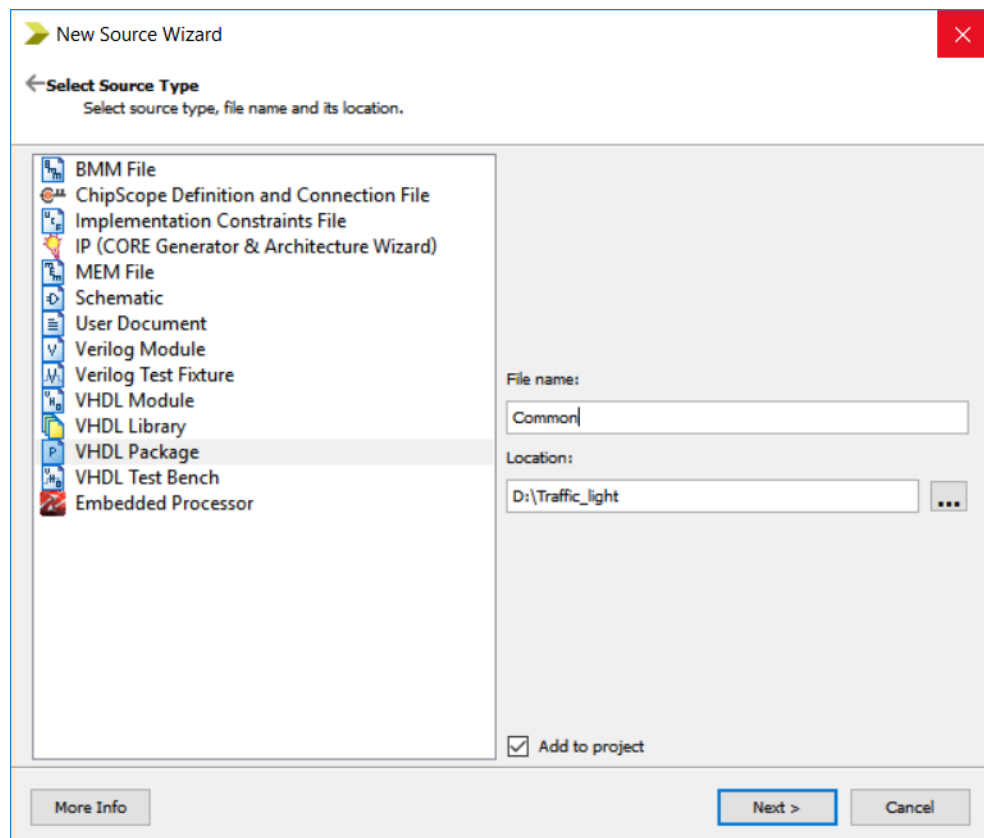- VHDL implementation
 - Create a Package for user defined types, constants and functions



VHDL FSM Implementation Example: Traffic Lights Control

- VHDL implementation
 - Create a Package for user defined types, constants and functions
 - traffic_light_state
 - S0: Initial
 - S1: Green
 - S2: Yellow
 - S3: Red
 - S4: Stop

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
  
package Common is  
type traffic_light_state is (S0, S1, S2, S3, S4);  
end Common;  
  
package body Common is  
end Common;
```

VHDL FSM Implementation Example: Traffic Lights Control

- VHDL implementation
 - Create a Package for user defined types, constants and functions
 - Use the package

```
use work.Common.all;
```

- Entity declaration

```
entity LightControl is
  Port ( I_EN      : in  STD_LOGIC;
         I_CLK     : in  STD_LOGIC;
         O_GREEN   : out STD_LOGIC;
         O_YELLOW  : out STD_LOGIC;
         O_RED     : out STD_LOGIC);
end LightControl;
```

VHDL FSM Implementation Example: Traffic Lights Control

- VHDL implementation
 - Architecture definition

```
architecture Behavioral of LightControl is
    signal state : traffic_light_state := S0;
begin
    process(I_CLK)
    begin
        if rising_edge(I_CLK) then
            if I_EN = '1' then
                if state = S0 then state <= S1;
                elsif state = S1 then state <= S2;
                elsif state = S2 then state <= S3;
                elsif state = S3 then state <= S1;
                end if;
            else
                if state = S0 then state <= S0;
                else state <= S4;
                end if;
            end if;
        end if;
    end process;
```

```
        process(state)
        begin
            if state = S1 then
                O_GREEN <= '1'; O_YELLOW <= '0'; O_RED <= '0';
            elsif state = S2 then
                O_GREEN <= '0'; O_YELLOW <= '1'; O_RED <= '0';
            elsif state = S3 then
                O_GREEN <= '0'; O_YELLOW <= '0'; O_RED <= '1';
            else
                O_GREEN <= '0'; O_YELLOW <= '0'; O_RED <= '0';
            end if;
        end process;
    end Behavioral;
```

VHDL FSM Implementation Example: Traffic Lights Control

- VHDL implementation: Testbench program

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

use work.Common.all;


ENTITY LightControl_test IS
END LightControl_test;

ARCHITECTURE behavior OF LightControl_test IS
    COMPONENT LightControl
    PORT (
        I_EN : IN  std_logic;
        I_CLK : IN  std_logic;
        O_GREEN : OUT std_logic;
        O_YELLOW : OUT std_logic;
        O_RED : OUT std_logic
    );
    END COMPONENT;
    signal I_EN : std_logic := '0';
    signal I_CLK : std_logic := '0';
    --Outputs
    signal O_GREEN : std_logic;
    signal O_YELLOW : std_logic;
    signal O_RED : std_logic;
    -- Clock period definitions
    constant I_CLK_period : time := 10 ns;
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
 uut: LightControl PORT MAP (
        I_EN => I_EN,
        I_CLK => I_CLK,
        O_GREEN => O_GREEN,
        O_YELLOW => O_YELLOW,
        O_RED => O_RED
    );
-- Clock process definitions
I_CLK_process :process
begin
    I_CLK <= '0';
    wait for I_CLK_period/2;
    I_CLK <= '1';
    wait for I_CLK_period/2;
end process;
-- Stimulus process
stim_proc: process
begin
    -- hold init state for 50 ns.
    wait for 50 ns;
    -- insert stimulus here
    I_EN <= '1'; wait for 300 ns;
    I_EN <= '0'; wait;
end process;
END;
```


VHDL FSM Implementation Example: Traffic Lights Control

 - VHDL implementation:
 - Simulation and waveforms



VHDL FSM Implementation Example: Traffic Lights Control

- State diagram with delays

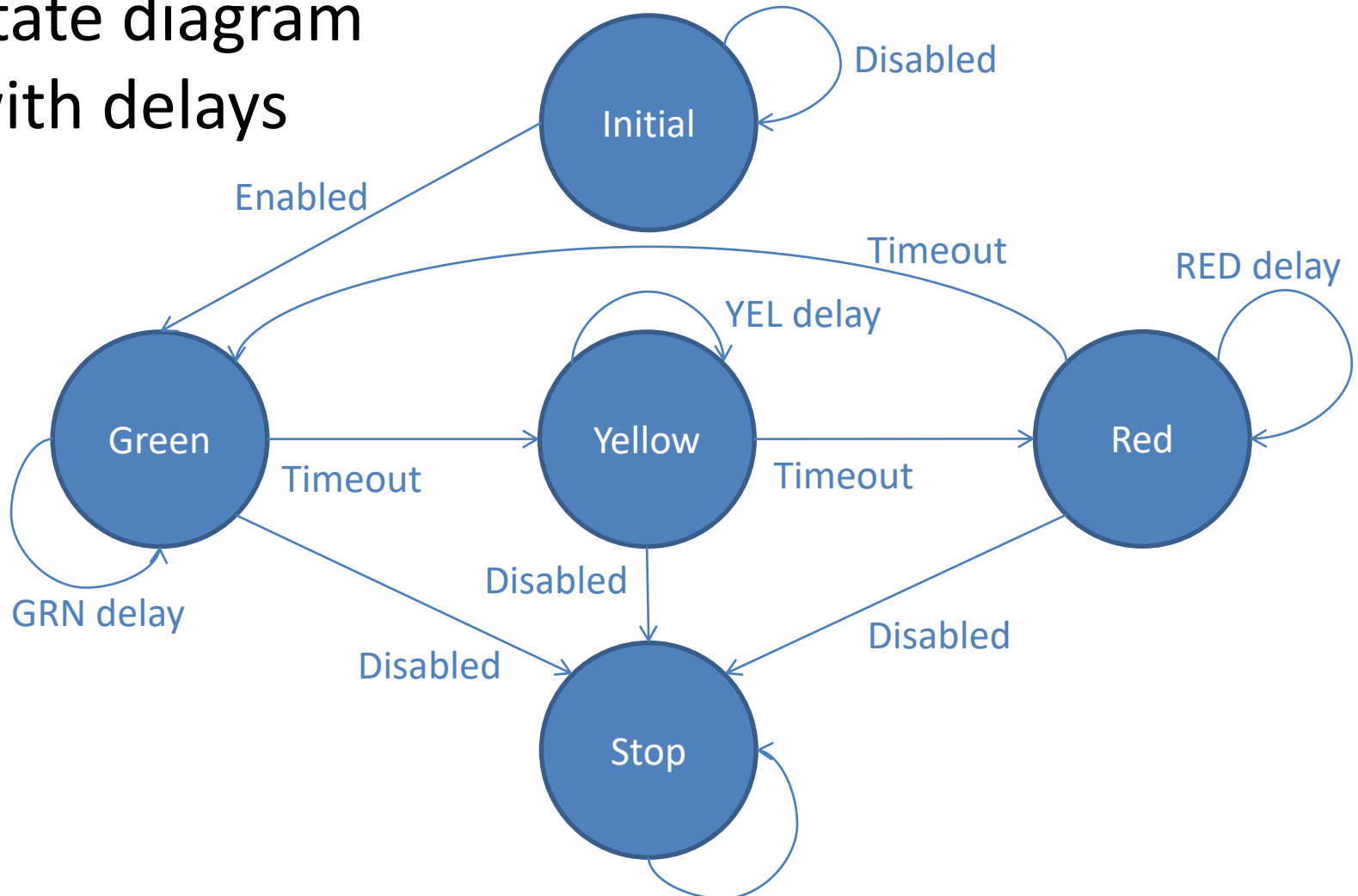

VHDL FSM Implementation Example: Traffic Lights Control

- VHDL implementation (with delay)
 - Create a Package for user defined types, constants and functions
 - traffic_light_state
 - S0: Initial
 - S1: Green
 - S2: Yellow
 - S3: Red
 - S4: Stop

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

package Common is
type traffic_light_state is (S0, S1, S2, S3, S4);
constant GRN_WAIT_CYCLES : integer := 5;
constant YEL_WAIT_CYCLES : integer := 2;
constant RED_WAIT_CYCLES : integer := 5;
end Common;

package body Common is
end Common;
```

VHDL FSM Implementation Example: Traffic Lights Control

- VHDL implementation (with delay)
 - Architecture definition (page 1)

```
15 architecture Behavioral of LightControlDelay is
16     signal state : traffic_light_state := S0;
17     signal counter_grn : integer := GRN_WAIT_CYCLES;
18     signal counter_yel : integer := YEL_WAIT_CYCLES;
19     signal counter_red : integer := RED_WAIT_CYCLES;
20 begin
21     process(I_CLK)
22     begin
23         if rising_edge(I_CLK) then
24             if I_EN = '1' then
25                 if state = S0 then
26                     state <= S1;
27                 elsif state = S1 then
28                     if counter_grn > 0 then
29                         counter_grn <= counter_grn-1;
30                     else
31                         state <= S2;
32                         counter_grn <= GRN_WAIT_CYCLES;
33                     end if;
```

```
34         elsif state = S2 then
35             if counter_yel > 0 then
36                 counter_yel <= counter_yel-1;
37             else
38                 state <= S3;
39                 counter_yel <= YEL_WAIT_CYCLES;
40             end if;
41         elsif state = S3 then
42             if counter_red > 0 then
43                 counter_red <= counter_red-1;
44             else
45                 state <= S1;
46                 counter_red <= RED_WAIT_CYCLES;
47             end if;
48         end if;
49     else
50         if state = S0 then state <= S0;
51         else state <= S4;
52         end if;
53     end if;
54 end if;
55 end process;
```

 

VHDL FSM Implementation Example: Traffic Lights Control

- VHDL implementation (with delay)
 - Architecture definition (page 2)

```
56
57     process(state)
58     begin
59         if state = S1 then
60             O_GREEN <= '1'; O_YELLOW <= '0'; O_RED <= '0';
61         elsif state = S2 then
62             O_GREEN <= '0'; O_YELLOW <= '1'; O_RED <= '0';
63         elsif state = S3 then
64             O_GREEN <= '0'; O_YELLOW <= '0'; O_RED <= '1';
65         else
66             O_GREEN <= '0'; O_YELLOW <= '0'; O_RED <= '0';
67         end if;
68     end process;
69 end Behavioral;
```


VHDL FSM Implementation Example: Traffic Lights Control

- VHDL implementation (with delay)
 - Simulation and waveforms



Homework


- Optimized Divider

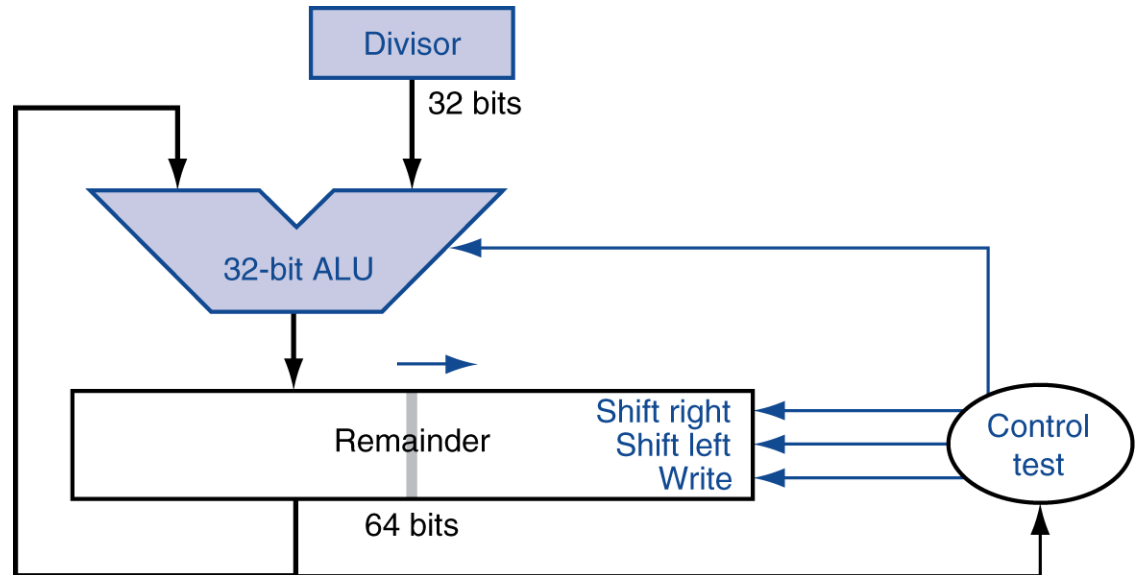

- N-bit division involves N steps
- Each step, the circuit is in one of the following states
 - Initial state
 - Shift state
 - Calculation state
 - Remainder update state
 - Stop

Homework


- Optimized Divider

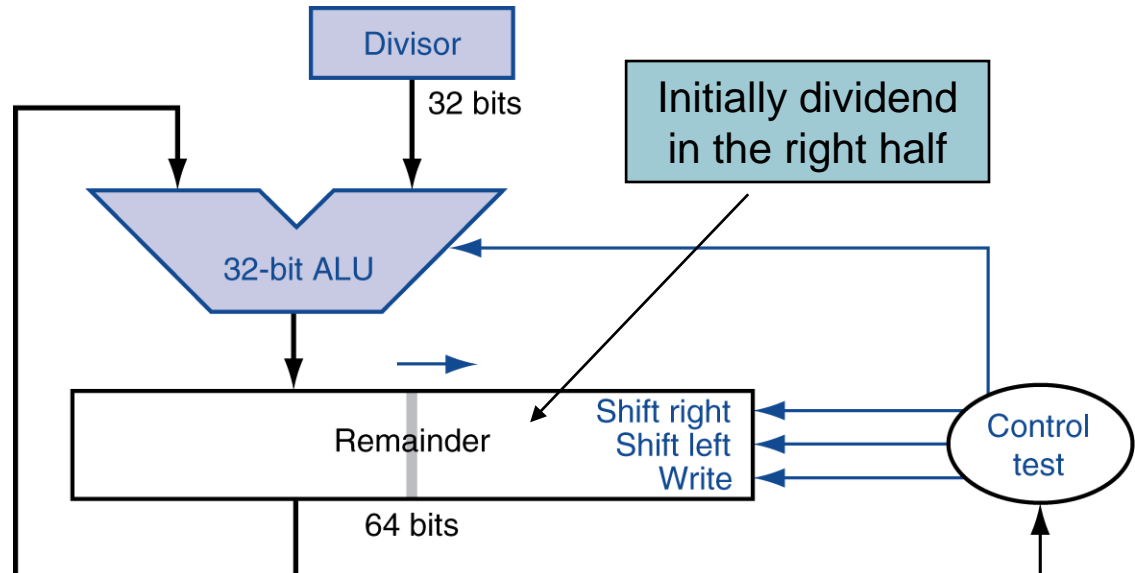

- The remainder register is double sized
 - Shift to left by 1 bit in each iteration
 - Only the higher half participates in subtraction
 - New quotient bit is shifted in from the right end
- In the end, the higher half is the remainder and the lower half is the quotient

Homework

- Optimized Divider

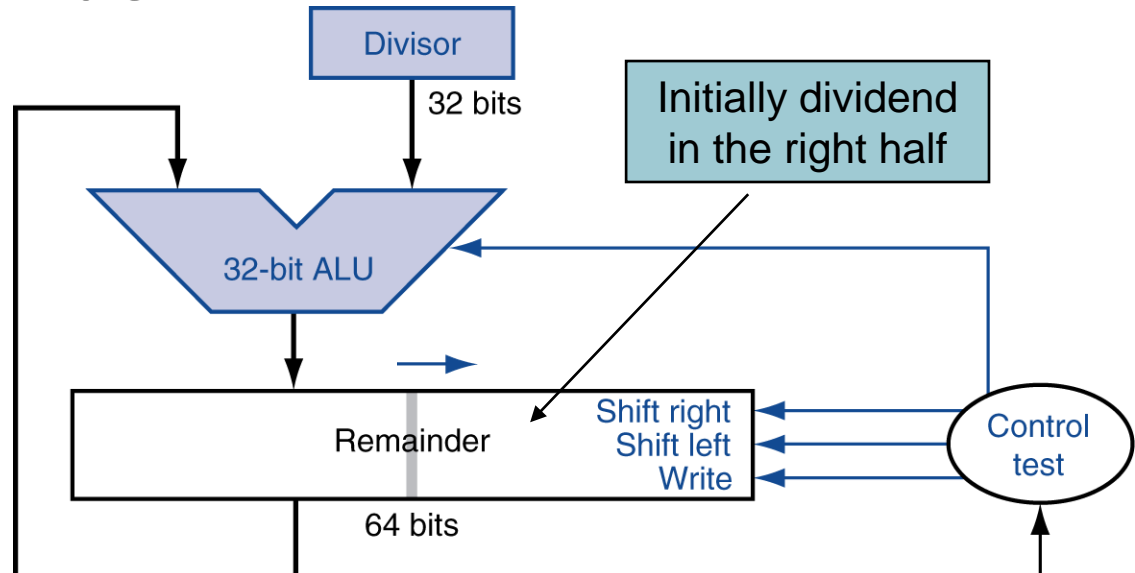


- The ALU

- Performs subtractions when enabled
- Can determine which operand is the bigger one
- Controlled by the control logic

Homework

- Optimized Divider

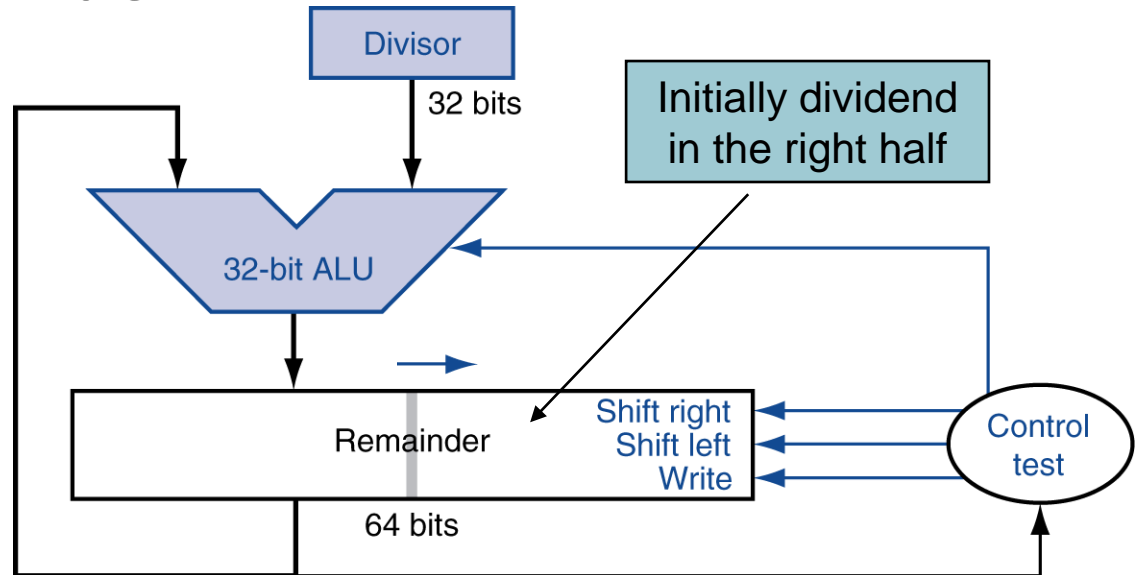

- The Control Unit

- Handles state transition
- Generate control signals
- Start and stop the calculation steps

